Download ISL Student Zone app from Playstore

Code No. 6066 / M

FACULTY OF ENGINEERING

B.E. 2/4 (M/P/CSE) II - Semester (Main) Examination, June 2014

Subject: Electrical Circuits & Machines

Time: 3 Hours


Max.Marks: 75

Note: Answer all questions from Part A. Answer any five questions from Part B. PART – A (25 Marks)

- State, explain Kirchoff's current law. 3 2 Write expressions for active and reactive power. 2 3 Explain how power is transformed from one circuit to another circuit in a 1-phase transformer. 3 4 What do you understand by balanced 3-phase circuits? 2 What are the conditions for self excitation in a D.C. shunt generator. 3 2 3 What do you understand by critical resistance in DC machine? 7 Draw speed-torque characteristics of an 3-phase insulation motor. Give reason why 3-phase induction motor cannot run at synchronous speed. 2 Why 1-phase induction motor are not self starting. 2 10 Calculate equivalent resistance between terminals A and B for the circuit shown below:
 - (All the values are in Ohms)

PART - B (50 Marks)

11.

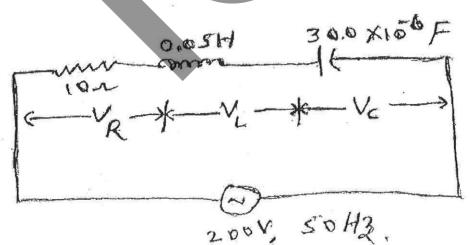

For the circuit shown above calculate Impedance, current, p-f, V_L , V_R , V_C , active power and reactive power. Also draw vector diagram.

10

Download ISL Student Zone app from Playstore

Code No. 6066 / 0

- 2 -

| 12 | 2 State and explain the following theorems | |
|-----------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|
| | a) Norton's theorem b) Thevanin's theorem. | |
| 13 | 3 (a) Prove that $V = \sqrt{3} V_{Ph}$ in 3-phase star connection. | 5 |
| | (b) The power in a 3-phase circuit is measured by two wattmeters. If the input power 100 kW and p.f. is 0.66 lagging. What will be the reading of each wattmeter? | is 5 |
| 14 | Explain in detail O.C and S.C. tests of a single-phase transformer with neat circ diagrams. Also explain how equivalent parameters and efficiency can be evaluated these tests. | uit by 10 |
| 15 | Explain in detail constructional details and principle operation of D.C. generator. Also | |
| | derive the emf equation of a D.C. machine. | so 10 |
| 16 | (a) Explain low production of rotating magnetic field is produced in 3-phase inducti motor. | |
| ę ^{ti} | (b) Explain any one method of starting of 3-phase induction motor with neat schema diagram. | 5 tic 5 |
| 17 | (a) Explain capacitor run motor with help of neat circuit diagram and mention application. | |
| e) | (b) Explain constructional details and working principle of stepper motor. | 5 5 |
| | | |
